# Laboratory Exercise 5

#### **Clocks and Timers**

This is an exercise in implementing and using a real-time clock.

#### Part I

Implement a 3-digit BCD counter. Display the contents of the counter on the 7-segment displays, HEX2-0. Derive a control signal, from the 50-MHz clock signal provided on the Altera DE2-115 board, to increment the contents of the counter at one-second intervals. Use the pushbutton switch KEY 0 to reset the counter to 0.

- 1. Create a new Quartus II project which will be used to implement the desired circuit on the DE2-115 board.
- 2. Write a Verilog file that specifies the desired circuit.
- 3. Include the Verilog file in your project and compile the circuit.
- 4. Simulate the designed circuit to verify its functionality.
- 5. Assign the pins on the FPGA to connect to the 7-segment displays and the pushbutton switch, as indicated in the User Manual for the DE2-115 board.
- 6. Recompile the circuit and download it into the FPGA chip.
- 7. Verify that your circuit works correctly by observing the display.

### Part II

Design and implement a circuit on the DE2-115 board that acts as a time-of-day clock. It should display the hour (from 0 to 23) on the 7-segment displays HEX7-6, the minute (from 0 to 60) on HEX5-4 and the second (from 0 to 60) on HEX3-2. Use the switches SW15-0 to preset the hour and minute parts of the time displayed by the clock.

## Part III

Design and implement on the DE2-115 board a reaction-timer circuit. The circuit is to operate as follows:

- 1. The circuit is reset by pressing the pushbutton switch KEY 0.
- 2. After an elapsed time, the red light labeled LEDR 0 turns on and a four-digit BCD counter starts counting in intervals of milliseconds. The amount of time in seconds from when the circuit is reset until LEDR 0 is turned on is set by switches SW7–0.
- 3. A person whose reflexes are being tested must press the pushbutton KEY 3 as quickly as possible to turn the LED off and freeze the counter in its present state. The count which shows the reaction time will be displayed on the 7-segment displays HEX2-0.

Copyright © 2010 Altera Corporation.